

# Harold's Flip-Flops Cheat Sheet



13 June 2020

S-R Flip-Flop (Edge-Triggered)																						
Style	NAND-NAND	AND-NOR																				
<b>Circuit</b>																						
<b>Symbol</b>	<p style="text-align: center;">(a) positive edge-triggered                      (b) negative edge-triggered</p>																					
<b>Truth Table</b>	<table border="1" style="margin-left: auto; margin-right: auto; border-collapse: collapse; text-align: center;"> <thead> <tr style="background-color: #f4a460;"> <th>S</th> <th>R</th> <th><math>Q_{next}</math></th> <th>Action</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q</td> <td>No change, Hold</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>Reset (<math>Q \rightarrow 0</math>)</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>Set (<math>Q \rightarrow 1</math>)</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>Invalid, Not allowed</td> </tr> </tbody> </table>		S	R	$Q_{next}$	Action	0	0	Q	No change, Hold	0	1	0	Reset ( $Q \rightarrow 0$ )	1	0	1	Set ( $Q \rightarrow 1$ )	1	1	X	Invalid, Not allowed
S	R	$Q_{next}$	Action																			
0	0	Q	No change, Hold																			
0	1	0	Reset ( $Q \rightarrow 0$ )																			
1	0	1	Set ( $Q \rightarrow 1$ )																			
1	1	X	Invalid, Not allowed																			
<b>Boolean Equation</b>	$Q_{next} = \bar{R}Q_{prev} + \bar{R}S = \bar{R}(Q_{prev} + S)$																					
<b>Name Origin</b>	SR for Set-Reset																					
<b>Observations</b>	A <b>Flip-Flop</b> is a <b>Latch</b> with 2 AND/NAND gates added for clock input to trigger data flow from left to right																					
<b>Applications</b>	<ul style="list-style-type: none"> <li>• Storing a single bit of data, 1 or 0</li> </ul>																					
<b>TTL Chips</b>	74x71, 74Lx74																					



## J-K Flip-Flop (Edge-Triggered)

Style	NAND-NAND	AND-NOR
-------	-----------	---------

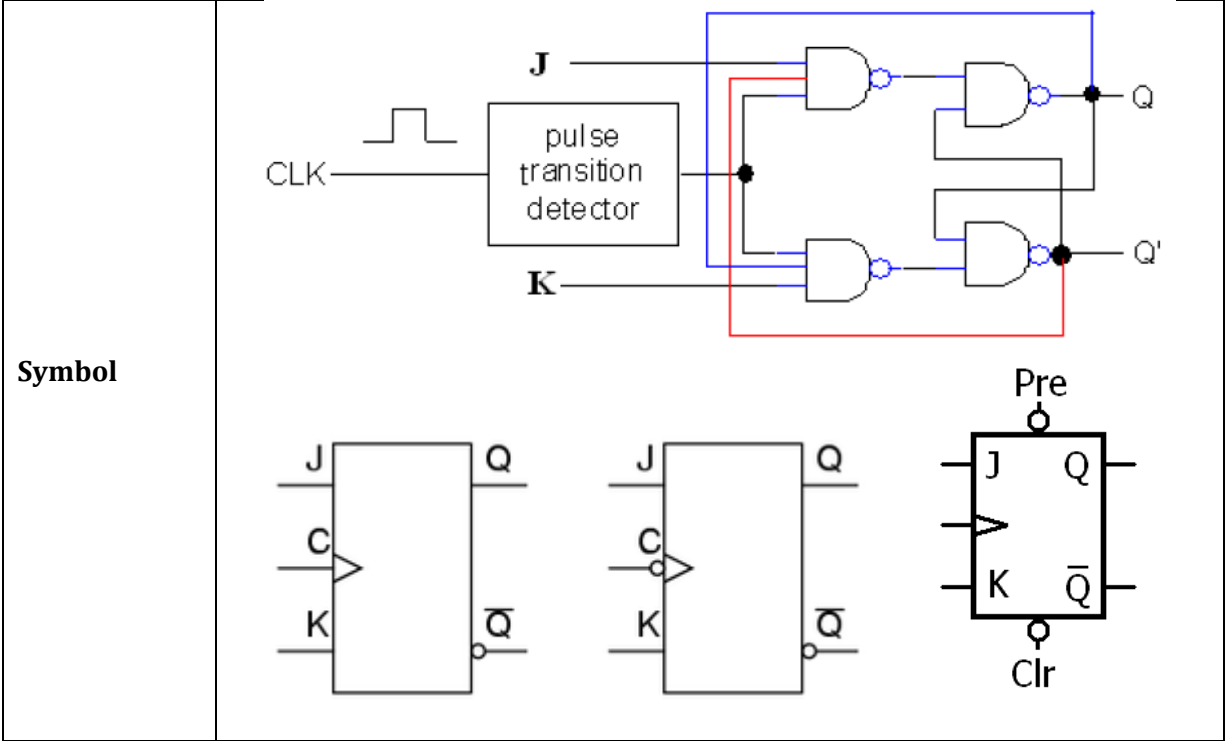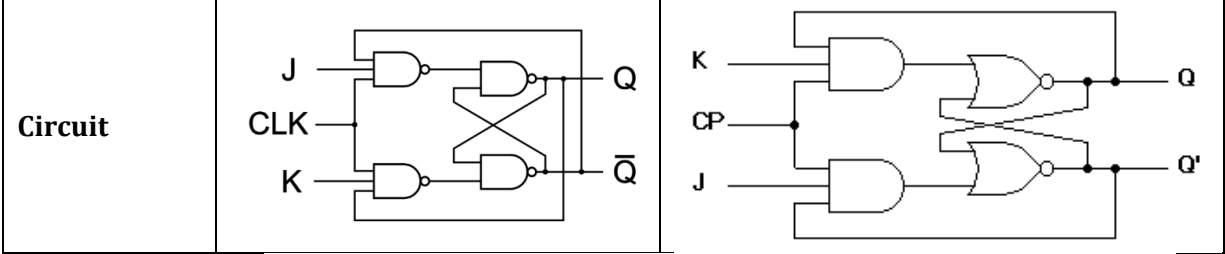

<b>Truth Table</b>	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr style="background-color: #e67e22; color: white;"> <th colspan="3">Inputs</th> <th colspan="2">Outputs</th> <th rowspan="2">Action</th> </tr> <tr style="background-color: #e67e22; color: white;"> <th>J</th> <th>K</th> <th>CLK</th> <th><math>Q_{next}</math></th> <th><math>Q'_{next}</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>↓</td> <td>Q</td> <td>Q'</td> <td>Hold, No change</td> </tr> <tr> <td>0</td> <td>1</td> <td>↓</td> <td>0</td> <td>1</td> <td>Reset (<math>Q \rightarrow 0</math>)</td> </tr> <tr> <td>1</td> <td>0</td> <td>↓</td> <td>1</td> <td>0</td> <td>Set (<math>Q \rightarrow 1</math>)</td> </tr> <tr> <td>1</td> <td>1</td> <td>↓</td> <td>Q'</td> <td>Q</td> <td>Toggle, Change (<math>1 \rightarrow 0</math>)</td> </tr> </tbody> </table>	Inputs			Outputs		Action	J	K	CLK	$Q_{next}$	$Q'_{next}$	0	0	↓	Q	Q'	Hold, No change	0	1	↓	0	1	Reset ( $Q \rightarrow 0$ )	1	0	↓	1	0	Set ( $Q \rightarrow 1$ )	1	1	↓	Q'	Q	Toggle, Change ( $1 \rightarrow 0$ )
Inputs			Outputs		Action																															
J	K	CLK	$Q_{next}$	$Q'_{next}$																																
0	0	↓	Q	Q'	Hold, No change																															
0	1	↓	0	1	Reset ( $Q \rightarrow 0$ )																															
1	0	↓	1	0	Set ( $Q \rightarrow 1$ )																															
1	1	↓	Q'	Q	Toggle, Change ( $1 \rightarrow 0$ )																															

<b>Boolean Equation</b>	$Q_{next} = J\bar{Q}_{prev} + \bar{K}Q_{prev}$
-------------------------	--

<b>Name Origin</b>	None, other than J and K are adjacent letters in the alphabet
--------------------	---

- |                     |  |
|---------------------|--|
| <b>Observations</b> | <ul style="list-style-type: none"> <li>Same as S-R flip-flop except 2 feedback lines added</li> <li>Fixes the invalid 1-1 state</li> </ul> |
|---------------------|--|

- |                     |   |
|---------------------|---|
| <b>Applications</b> | <ul style="list-style-type: none"> <li><u>Frequency Division</u>: If <math>J = K = \text{HIGH}</math>, then clock frequency divider (<math>f/2</math>)</li> <li><u>Counting</u>: If cascaded with <math>Q_A</math> wired to <math>JK_B</math> CLK, then <math>Q_A = \text{LSB}</math> and <math>Q_B = \text{MSB}</math></li> <li><u>Sequence Detection</u>: If cascaded with <math>Q_A \rightarrow J_B</math> and <math>Q'_A \rightarrow K_B</math>, then tap Q/Q's for 1/0 pattern, then AND for output</li> </ul> |
|---------------------|---|

<b>TTL Chips</b>	74x68, 74x69, 74x70, 74x73, 74x76, 74x101, 74x102, 74x103, 74x107
------------------	---


## T Flip-Flop (Edge-Triggered)

Style	NAND-NAND	AND-NOR																				
<b>Circuit</b>																						
<b>Symbol</b>																						
<b>Truth Table</b>	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th colspan="2">Inputs</th> <th colspan="2">Outputs</th> <th rowspan="2">Action</th> </tr> <tr> <th>T</th> <th>CLK</th> <th><math>Q_{next}</math></th> <th><math>Q'_{next}</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>↑</td> <td>Q</td> <td>Q'</td> <td>No change, Hold</td> </tr> <tr> <td>1</td> <td>↑</td> <td>Q'</td> <td>Q</td> <td>Change, Toggle</td> </tr> </tbody> </table>			Inputs		Outputs		Action	T	CLK	$Q_{next}$	$Q'_{next}$	0	↑	Q	Q'	No change, Hold	1	↑	Q'	Q	Change, Toggle
Inputs		Outputs		Action																		
T	CLK	$Q_{next}$	$Q'_{next}$																			
0	↑	Q	Q'	No change, Hold																		
1	↑	Q'	Q	Change, Toggle																		
<b>Boolean Equation</b>	$Q_{next} = \bar{Q}_{prev}$																					
<b>Name Origin</b>	T for <u>T</u> oggle, since it changes state on the triggering edge of the clock pulse																					
<b>Observations</b>	<ul style="list-style-type: none"> <li>Made with J-K flip-flop with input T connected to both J and K</li> <li>Implements the two middle rows of the J-K flip-flop truth table</li> </ul>																					
<b>Applications</b>	<ul style="list-style-type: none"> <li><u>Frequency Division</u>: If J = K = HIGH, then clock frequency divider (<math>f/2</math>)</li> </ul>																					
<b>TTL Chips</b>	74x374 or use J-K flip-flop chips																					

## J-K Flip-Flop Applications

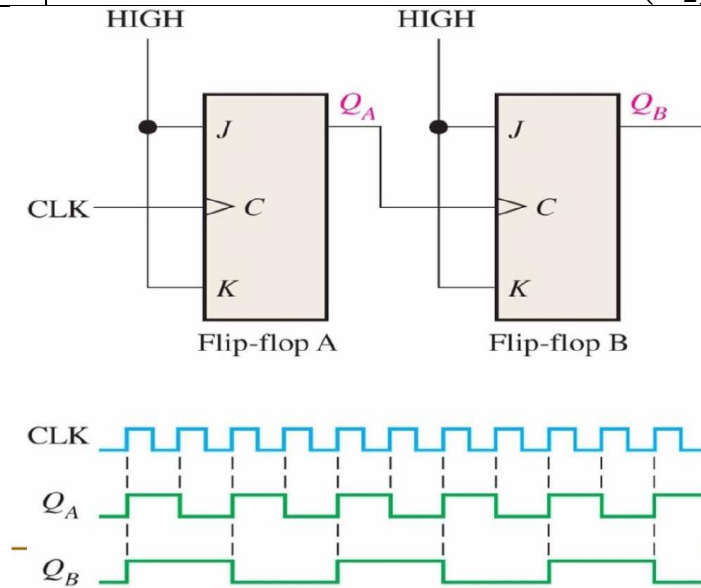
### Frequency Division


If  $J = K = \text{HIGH}$ , then clock frequency divider ( $f/2$ )


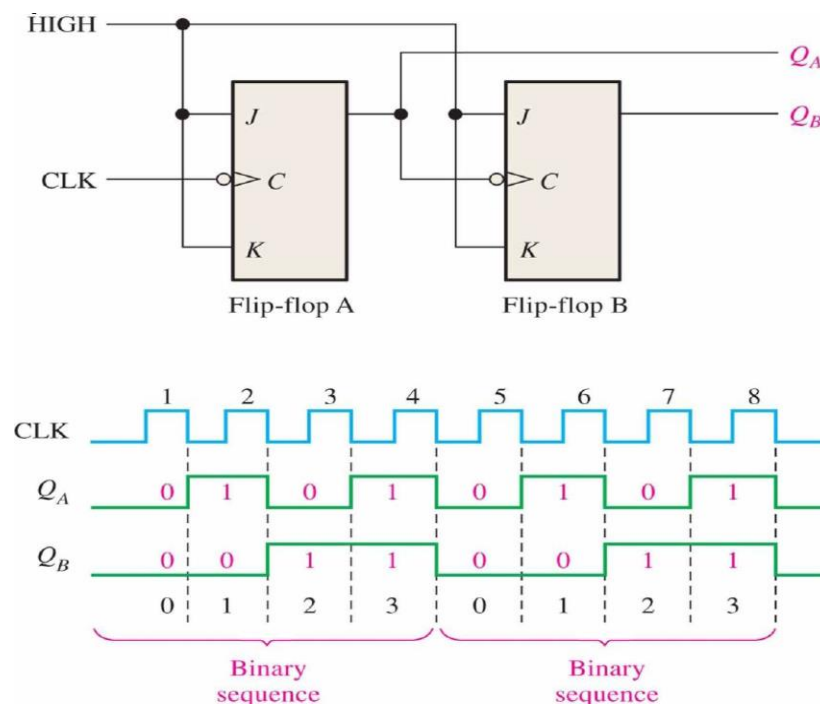
### Counting

If cascaded with  $Q_A$  wired to  $J_{K_B}$  CLK, then  $Q_A = \text{LSB}$  and  $Q_B = \text{MSB}$



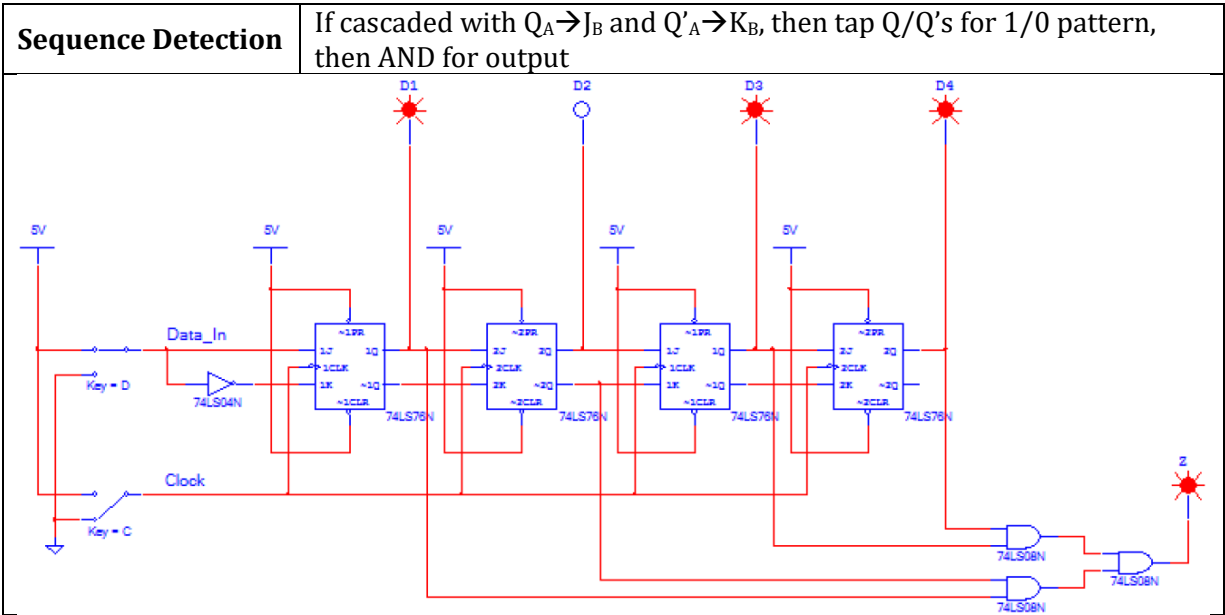

Credit: Diagrams taken from “ECPI University EET 230 – Digital Systems II”, Wikipedia, and Google images.