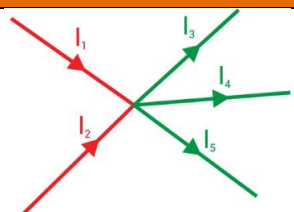
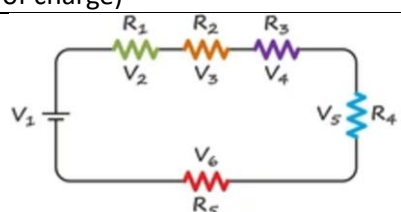
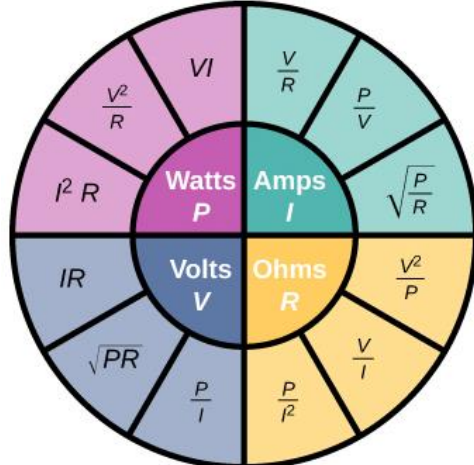


Harold's AC Circuits








Cheat Sheet

2 December 2024

Circuit Laws

Circuit Law	Formula	
Kirchhoff's Current Law (KCL)	$\sum_{i=1}^n I_i = 0$ $I_{in1} + I_{in2} = I_{out1} + I_{out2} + I_{out3}$	
	The total current flowing into a node or junction must equal the total current flowing out of the node or junction. (conservation of charge)	
Kirchhoff's Voltage Law (KVL)	$\sum_{i=1}^n V_i = 0$ $V_1 = V_2 + V_3 + V_4 + V_5 + V_6$	
	The sum of all voltages around a circuit loop is equal to zero. (conservation of energy)	
Ohm's Law	$V = IR \text{ (DC circuit)}$ $V = IZ_{Eq} \text{ (AC circuit)}$	
Power	$P = VI$ $P = I^2 R$ $P = \frac{V^2}{R}$ $P = \frac{W}{t}$	An across (V) times a through (I) variable. $\text{Watt (W)} = \frac{\text{Volt (V)}}{\text{Ampere (A)}}$
Electrical Energy	$E = QV$ $E = VIt$ $P = I^2 Rt$ $E = Pt$	$\text{Joule (J)} = \frac{\text{Watt (W)}}{\text{second (s)}}$

Components in Series/Parallel

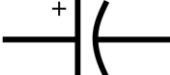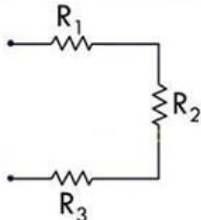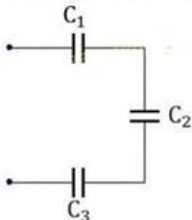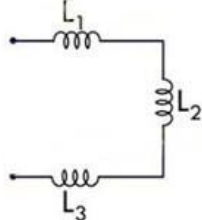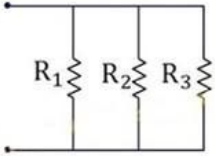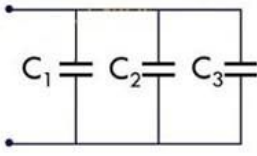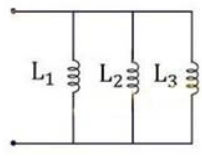Element	Resistor	Capacitor	Inductor
Component			
Symbol			
Denoted by	R	C	L
Units	Ω (Ohm)	F (Farad)	H (Henry)
Equation	$R = \frac{V_R}{I}$	$C = \frac{Q}{V_C}$	$L = \frac{V_L}{\left(\frac{di}{dt}\right)}$
Series			
	$R_T = R_1 + R_2 + R_3$	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$	$L_T = L_1 + L_2 + L_3$
Parallel			
	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$	$C_T = C_1 + C_2 + C_3$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$


Impedance

Component	Units	Impedance (Z)	Phasor Notation	Complex Notation
Resistance (R)	Ω (Ohm)	$Z_R = R$	$R \angle 0^\circ$	$R + 0j$
Inductance (L)	mH (Henry)	$Z_L = j\omega L$	$ Z_L \angle 90^\circ$	$0 + Z_L j$
Capacitance (C)	μF (Farad)	$Z_C = \frac{1}{j\omega C} = -j\frac{1}{\omega C}$	$ Z_C \angle -90^\circ$	$0 - Z_C j$
Impedance (Z)	Ω (Ohm)	$Z_{eq} = Z_R + Z_L + Z_C$	$ Z_{eq} \angle \theta^\circ$	$Z_{Re} + Z_{Im}j$
Alternating Voltage (V)	V (Volts)	$V = IZ_{eq}$	$ V_{eq} \angle \theta^\circ$	$V_{Re} + V_{Im}j$
Alternating Current (I)	A (Ampere)	$I_{eq} = \frac{V}{Z_{eq}}$	$ I_{eq} \angle \theta^\circ$	$I_{Re} + I_{Im}j$
NOTE: In circuits, j is used to denote $\sqrt{-1}$ instead of i , which is already used for current.				


Phasor Math

Circuit Law	Formula	TI-84 Calculator
Phasor (Polar)	$ Z \angle \theta^\circ = Z e^{\theta j}$ $80 \angle -30^\circ = 80e^{-30j}$	<i>Example: $80 \angle -30^\circ$</i> [MODE] RADIAN [MODE] $re^{(\theta i)}$ [2 nd] [QUIT] [8] [0] [2 nd] [e ^x] [-] [3] [0] [2 nd] [π] [$\div$] [180] [2 nd] [i] [ENTER]
Complex (Rectangular)	$Z_{Re} + Z_{Im}j$	<i>Example: $2 + 3i$</i> [MODE] DEGREE [MODE] a+bi [2 nd] [QUIT] [2]+[3][2 nd] [i] [ENTER]
Addition	$ Z_1 \angle \theta_1^\circ + Z_2 \angle \theta_2^\circ$ 1. Convert from polar to rectangular form 2. Add real to real and imaginary to imaginary 3. Convert back from rectangular to polar form	
Division	$\frac{ Z_1 \angle \theta_1^\circ}{ Z_2 \angle \theta_2^\circ} = \left \frac{Z_1}{Z_2} \right \angle (\theta_1^\circ - \theta_2^\circ)$	
Rectangular → Polar	$Z = Z_{Re} + Z_{Im}j \rightarrow Z \angle \theta$ $ Z = \sqrt{Z_{Re}^2 + Z_{Im}^2}$ $\theta = \tan^{-1} \left(\frac{Z_{Im}}{Z_{Re}} \right)$	<i>Example: $2 + 3i$</i> [MODE] DEGREE [MODE] $re^{(\theta i)}$ [2 nd] [QUIT] [2] + [3] [2 nd] [i] [ENTER] [ANS] = $3.61e^{56.31i}$ [2] + [3] [2 nd] [i] [ENTER] [MATH][CPX][$\blacktriangleright$ Polar] [ENTER]
Polar → Rectangular	$Z = Z \angle \theta \rightarrow Z_{Re} + Z_{Im}j$ $Z_{Re} = Z \cos(\theta)$ $Z_{Im} = Z \sin(\theta)$	<i>Example: $80 \angle -30^\circ$</i> [MODE] RADIAN [MODE] a+bi [2 nd] [QUIT] 8 [0] [2 nd] [e ^x] [-] [3] [0] [2 nd] [π] [$\div$] [180] [2 nd] [i] [ENTER] [ANS] = $69.28 - 40i$ 8 [0] [2 nd] [e ^x] [-] [3] [0] [2 nd] [π] [$\div$] [180] [2 nd] [i] [ENTER] [MATH][CPX][$\blacktriangleright$ Rect] [ENTER]

Resonance

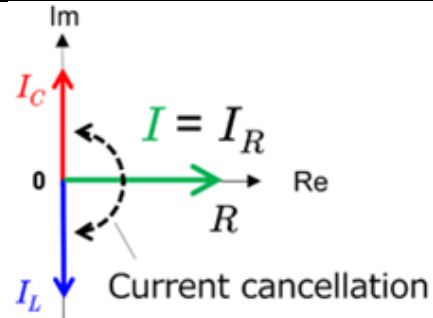Term	Formula	TI-84 Calculator
Frequency (Hz)	$\omega = 2\pi f$ $\frac{\omega^\circ}{\text{sec}} = \omega \left(\frac{\pi}{180^\circ} \right) \frac{\text{rad}}{\text{sec}}$	[MODE] DEGREE [MODE] RADIAN
Resonance Frequency	$Z_L + Z_C = 0$ $\omega_0 = \frac{1}{\sqrt{LC}} \frac{\text{rad}}{\text{s}}$ $f_0 = \frac{1}{2\pi\sqrt{LC}} \text{Hz}$	

AC Circuit Example #1: Series RLC

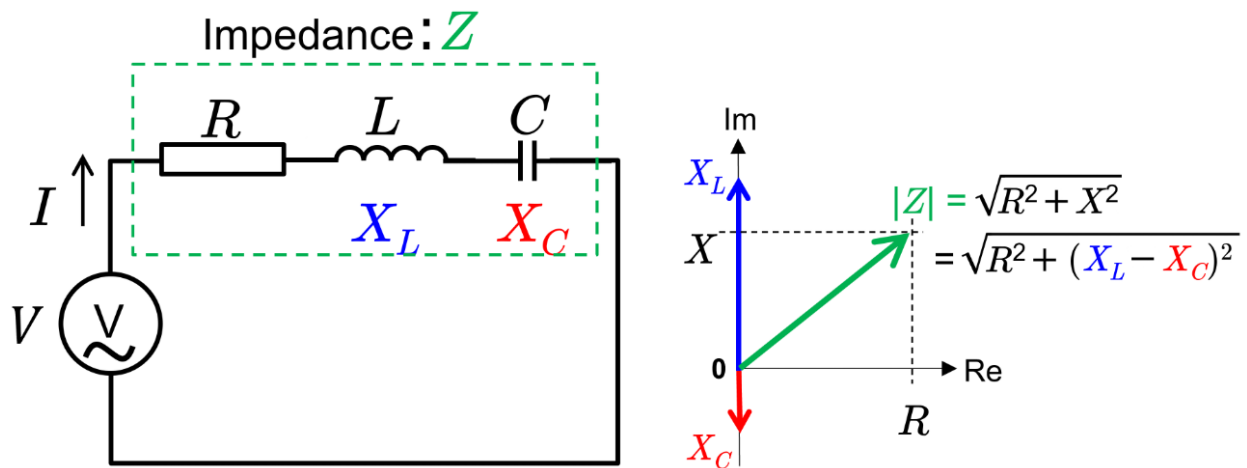


$$V = Z_{eq}I$$

$$V = (Z_R + Z_L + Z_C)I$$

$$V = \left(R + j\omega L + \frac{1}{j\omega C}\right)I = \left(R + j\omega L - j\frac{1}{\omega C}\right)I$$


AC Circuit Example #2: Parallel RLC

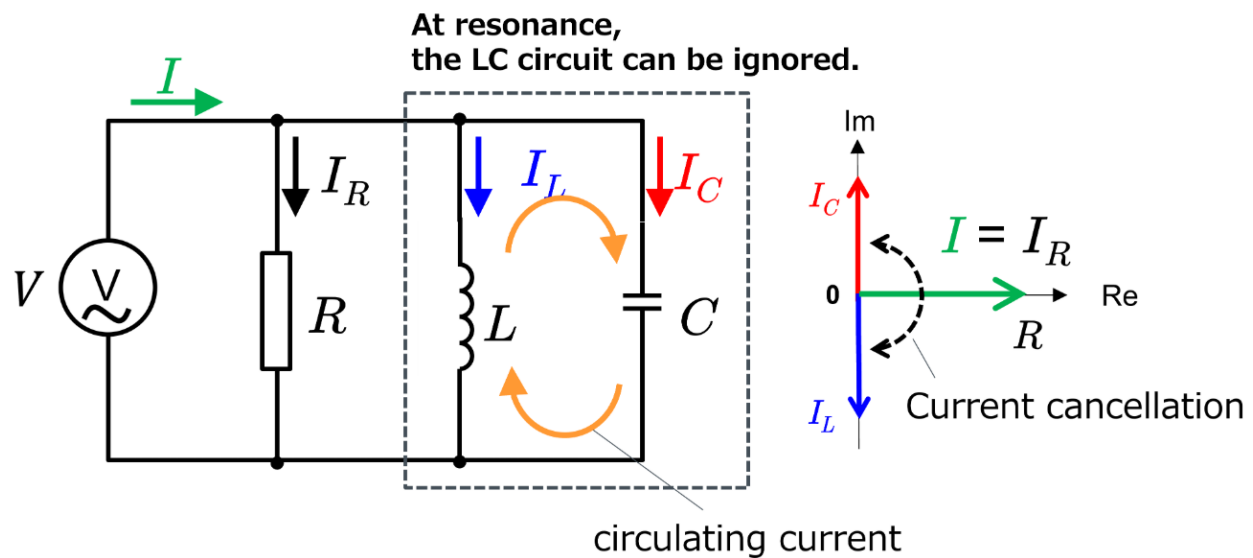

$$V = Z_{eq}I$$

$$V = \left(\frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}}\right)I = \left(\frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C}\right)I$$

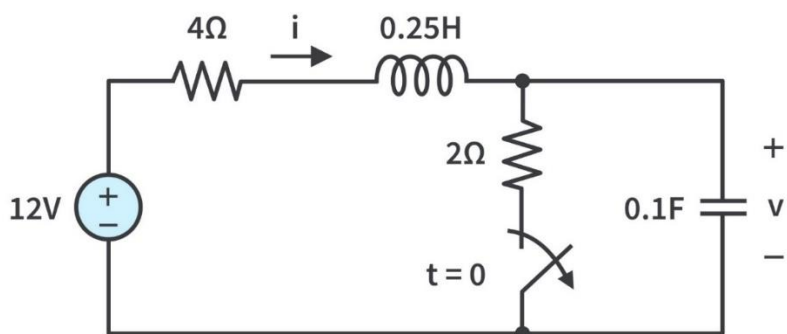AC Circuit Example #3: Series (RL) and Parallel (RC)



1. Determine the impedance from series and parallel components using complex notation.

$$Z_{eq} = (Z_{R1} + Z_L) + \left(\frac{1}{\frac{1}{Z_{R2}} + \frac{1}{Z_C}} \right)$$

$$Z_{eq} = (R_1 + j\omega L) + \left(\frac{1}{\frac{1}{R_2} + \frac{1}{j\omega C}} \right)$$

2. Substitute values.

$$Z_{eq} = (4 + (0.25)(10^{-3})\omega j) + \left(\frac{1}{\frac{1}{2} - (0.1)(10^{-6})\omega j} \right)$$

$$Z_{eq} = (4 + 2.5 \cdot 10^{-4}\omega j) + \left(\frac{1}{0.5 - 10^{-7}\omega j} \right)$$

$$Z_{eq} = (4 + 2.5 \cdot 10^{-4}\omega j) + \left(\frac{0.5}{0.25 + 10^{-14}\omega^2} + \frac{10^{-7}\omega}{0.25 + 10^{-14}\omega^2}j \right)$$

$$Z_{eq} = \left(4 + \frac{0.5}{0.25 + 10^{-14}\omega^2} \right) + \left(2.5 \cdot 10^{-4}\omega + \frac{10^{-7}\omega}{0.25 + 10^{-14}\omega^2} \right)j$$

3. Convert from complex to polar notation.

$$Z_{eq} = Z_{Re} + Z_{Im}j$$

$$Z_{Re} = \left(4 + \frac{0.5}{0.25 + 10^{-14}\omega^2} \right)$$

$$Z_{Im} = \left(2.5 \cdot 10^{-4}\omega + \frac{10^{-7}\omega}{0.25 + 10^{-14}\omega^2} \right)$$

$$|Z_{eq}| = \sqrt{Z_{Re}^2 + Z_{Im}^2}$$

$$\theta = \tan^{-1} \left(\frac{Z_{Im}}{Z_{Re}} \right)$$

$$Z_{eq} = |Z_{eq}| \angle \theta$$

Sources:

- Electrical Technology (2020 Oct). Resistance, Capacitance & Inductance in Series-Parallel – Equation & Formulas. <https://www.electricaltechnology.org/2020/10/resistance-inductance-capacitance-series-parallel-formulas.html>
- LibreTexts Physics (2024). 9.6: Electrical Energy and Power. [https://phys.libretexts.org/Bookshelves/University_Physics/University_Physics_\(OpenStax\)/University_Physics_II_-_Thermodynamics_Electricity_and_Magnetism_\(OpenStax\)/09%3A Current and Resistance/9.06%3A Electrical Energy and Power](https://phys.libretexts.org/Bookshelves/University_Physics/University_Physics_(OpenStax)/University_Physics_II_-_Thermodynamics_Electricity_and_Magnetism_(OpenStax)/09%3A_Current_and_Resistance/9.06%3A_Electrical_Energy_and_Power)
- Tech Web (2024). Resonant Circuits: Resonant Frequency and Q Factor. <https://techweb.rohm.com/product/power-device/si/18332/>